

Logic Gates: Explanation, Conversion & Formulas

Logic Gates Concepts & Formulas

1. AND Gate:

- Symbol: $A * B$
- Output is 1 only when both inputs are 1.

Truth Table:

A	B	A AND B
---	---	---------

0	0	0
---	---	---

0	1	0
---	---	---

1	0	0
---	---	---

1	1	1
---	---	---

2. OR Gate:

- Symbol: $A + B$
- Output is 1 when any input is 1.

3. NOT Gate:

- Symbol: A' or \bar{A}
- Output is opposite of input.

4. NAND Gate:

- Formula: $(A * B)'$
- Opposite of AND gate.

5. NOR Gate:

- Formula: $(A + B)'$
- Opposite of OR gate.

6. XOR Gate (Exclusive OR):

- Formula: $A \text{ XOR } B = A'B + AB'$

Logic Gates: Explanation, Conversion & Formulas

- Output is 1 when inputs are different.

7. XNOR Gate (Exclusive NOR):

- Formula: $A \text{ XOR } B' = AB + A'B'$
- Output is 1 when inputs are same.

Gate Conversion Using NAND:

- NOT: $A \text{ NAND } A = A'$
- AND: $(A \text{ NAND } B)' = A * B$
- OR: $A \text{ OR } B = (A' * B')'$

Gate Conversion Using NOR:

- NOT: $A \text{ NOR } A = A'$
- OR: $(A \text{ NOR } B)' = A + B$
- AND: $A \text{ AND } B = (A' + B')'$

Boolean Algebra Laws:

- Identity: $A + 0 = A$, $A * 1 = A$
- Null: $A + 1 = 1$, $A * 0 = 0$
- Inverse: $A + A' = 1$, $A * A' = 0$
- De Morgan's: $(AB)' = A' + B'$, $(A + B)' = A' * B'$